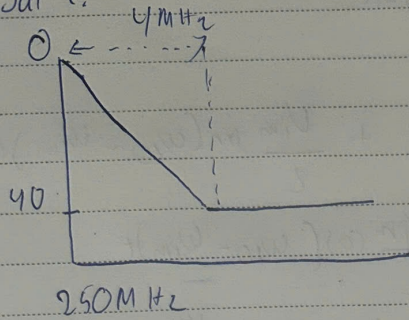


Bài 1:



$$\Delta A = -40 \text{ dB}$$

$$\Delta f = \log_{10} \left( \frac{254}{250} \right) \approx 0,007$$

$$\Rightarrow \text{Độ dốc} = \frac{-40}{0,007} = -5700 \text{ dB/decade}$$

$$A(f) = 10 \log_{10} \left( 1 + \left( \frac{f}{f_c} \right)^{2n} \right)$$

$$A = 40 \text{ dB}$$


$$\frac{f}{f_c} = \frac{254}{250} = 1,016$$

$$\Rightarrow 40 = 10 \log_{10} (1 + 1,016^{2n})$$

$$\Rightarrow n \approx 290$$

bộ lọc bậc cao

Bài 2:

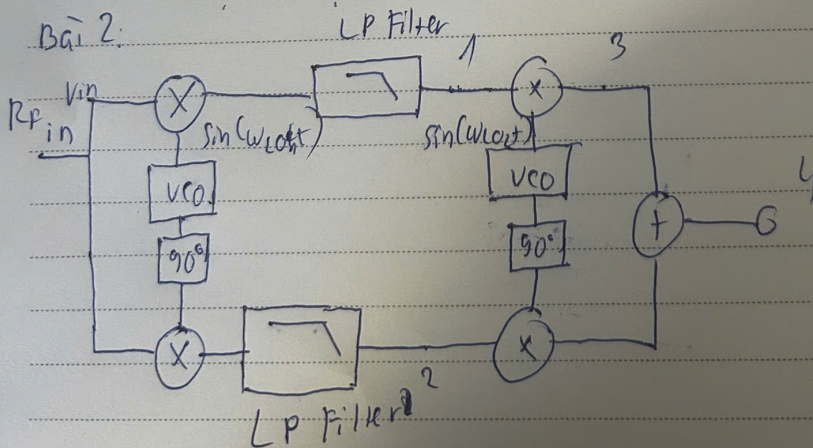

$$V_{in} = V_{RF} \cos \omega_{RF} t + V_{im} \cos \omega_{im} t$$

$$\omega_{RF} > \omega_{LO}$$

$$V_{in} = \frac{V_{RF}}{2} \sin(\omega_{RF} - \omega_{LO})t + \frac{V_{im}}{2} \sin(\omega_{LO} - \omega_{im})t$$

$$V_2 = \frac{V_{RF}}{2} \cos(\omega_{RF} - \omega_{LO})t + \frac{V_{im}}{2} \cos(\omega_{LO} - \omega_{im})t$$

$$V_3 = \frac{V_{RF}}{4} \cos(\omega_{RF} - \omega_{LO1} - \omega_{LO2})t - \frac{V_{im}}{4} \cos(\omega_{LO1} - \omega_{im} - \omega_{LO2})t$$

Ngõ ra nhánh dưới =

$$\frac{V_{RF}}{4} \cos(\omega_{RF} - \omega_{LO1} - \omega_{LO2})t + \frac{V_{im}}{4} \cos(\omega_{LO1} - \omega_{im} - \omega_{LO2})t$$

$$V_4 = \frac{V_{RF}}{2} \cos(\omega_{RF} - \omega_{LO1} - \omega_{LO2})t = V_{out}$$